

Inputs				Selection lines		Expected Output
$x_0$	$x_1$	$x_2$	$x_3$	$C_1$	$C_0$	$M$
0	0	0	0	0	0	0
0	1	0	0	0	1	1
1	0	1	0	1	0	1
1	1	1	1	1	1	1
0	1	1	0	1	0	1

If we take selection lines 0 0 the Expected output is 0 (which is equivalent to  $x_0$ )

For 0 1 the expected output is 1 (equivalent to  $x_1$ )

For 1 0 the expected output is 1 (equivalent to  $x_2$ )

For 1 1 the expected output is 1 (equivalent to  $x_3$ )

For 1 0 the expected output is 1 (equivalent to  $x_2$ )